

P1.6-1

$$\text{a.) } q = \int i dt = i\Delta t = (10 \text{ A})(2 \text{ hrs})(3600 \text{ s/hr}) = \underline{7.2 \times 10^4 \text{ C}}$$

$$\text{b.) } P = vi = (110 \text{ V})(10 \text{ A}) = \underline{1100 \text{ W}}$$

$$\text{c.) } \text{Cost} = \frac{0.06 \text{ \$}}{\text{kWhr}} \times 1.1 \text{ kW} \times 2 \text{ hrs} = \underline{0.132 \text{ \$}}$$

P1.6-2

$$P = (6 \text{ V})(10 \text{ mA}) = 0.06 \text{ W}$$

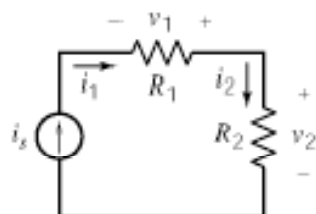
$$\Delta t = \frac{\Delta w}{P} = \frac{200 \text{ W}\cdot\text{s}}{0.06 \text{ W}} = \underline{3.33 \times 10^3 \text{ s}}$$

VP 1-1

Notice that the element voltage and current of each branch adhere to the passive convention. The sum of the powers absorbed by each branch are:

$$(-2 \text{ V})(2 \text{ A}) + (5 \text{ V})(2 \text{ A}) + (3 \text{ V})(3 \text{ A}) + (4 \text{ V})(-5 \text{ A}) + (1 \text{ V})(5 \text{ A}) = -4 \text{ W} + 10 \text{ W} + 9 \text{ W} - 20 \text{ W} + 5 \text{ W} = 0 \text{ W}$$

The element voltages and currents satisfy conservation of energy and may be correct.

P2.5-6

$$i_1 = i_2 = i_s = 2 \text{ A};$$

$$R_1 = 4 \Omega \text{ and } R_2 = 8 \Omega$$

v_1 and i_1 do not adhere to the passive convention so

$$v_1 = -R_1 i_1 = -4 \cdot 2 = \underline{-8 \text{ V}}$$

The power absorbed by R_1 is

$$P_1 = -v_1 i_1 = -(-8)(2) = \underline{16 \text{ W}}$$

v_2 and i_2 do adhere to the passive convention so $v_2 = R_2 i_2 = 8 \cdot 2 = \underline{16 \text{ V}}$.

The power absorbed by R_2 is $P_2 = v_2 i_2 = 16 \cdot 2 = \underline{32 \text{ W}}$.

P2.5-7

Model the heater as a resistor, then

$$\text{with a } 250 \text{ V source: } P = \frac{v^2}{R} \Rightarrow R = \frac{v^2}{P} = \frac{(250)^2}{1000} = \underline{62.5 \Omega}$$

$$\text{with a } 210 \text{ V source: } P = \frac{v^2}{R} = \frac{(210)^2}{62.5} = \underline{705.6 \text{ W}}$$

P2.6-2

(a) $v = R i_s = 5 \cdot 2 = \underline{10 \text{ V}}$ and $P = \frac{v^2}{R} = \frac{10^2}{5} = \underline{20 \text{ W}}$

(b) v and P do not depend on v_s .

The values of v and P are 10V and 20 W both when $v_s = 10 \text{ V}$ and when $v_s = 5 \text{ V}$

P2.6-3

Consider the current source:

i_s and v_s do not adhere to the passive convention,

so $P_{cs} = i_s v_s = 3 \cdot 12 = \underline{36 \text{ W}}$

is the power supplied by the current source.




Consider the voltage source:

i_s and v_s do adhere to the passive convention,


so $P_w = i_s v_s = 3 \cdot 12 = \underline{36 \text{ W}}$

is the power absorbed by the voltage source.

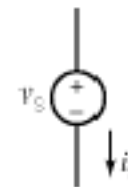\therefore The voltage source supplies -36 W .



P3.3-1

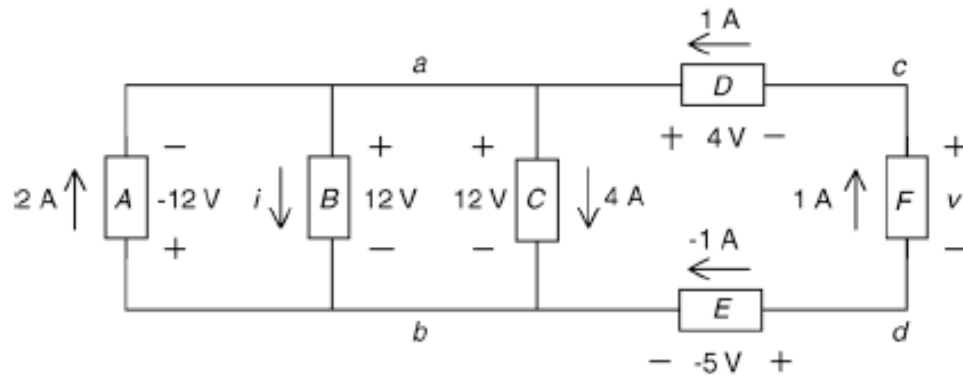

Apply KCL at node a to get $2 + 1 = i + 4 \Rightarrow i = -1 \text{ A}$

The current and voltage of element B adhere to the passive convention so $(12)(-1) = -12 \text{ W}$ is power received by element B . The power supplied by element B is 12 W.

Apply KVL to the loop consisting of elements $D, F, E,$ and C to get


$$4 + v + (-5) - 12 = 0 \Rightarrow v = 13 \text{ V}$$

The current and voltage of element F do not adhere to the passive convention so $(13)(1) = 13 \text{ W}$ is the power supplied by element F .

Check: The sum of the power supplied by all branches is

$$-(2)(-12) + 12 - (4)(12) + (1)(4) + 13 - (-1)(-5) = 24 + 12 - 48 + 4 + 13 - 5 = 0$$

P3.3-2

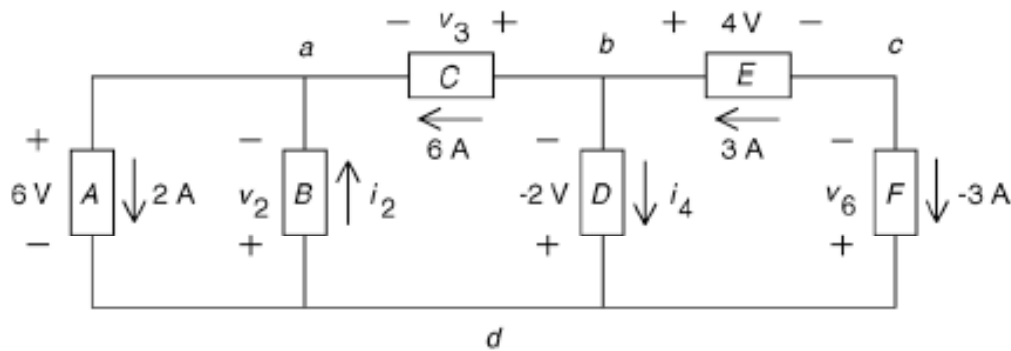

Apply KCL at node a to get $2 = i_2 + 6 = 0 \Rightarrow i_2 = -4 \text{ A}$

Apply KCL at node b to get $3 = i_4 + 6 \Rightarrow i_4 = -3 \text{ A}$

Apply KVL to the loop consisting of elements A and B to get

$$-v_2 - 6 = 0 \Rightarrow v_2 = -6 \text{ V}$$

Apply KVL to the loop consisting of elements C , D , and A to get

$$-v_3 - (-2) - 6 = 0 \Rightarrow v_3 = -4 \text{ V}$$


Apply KVL to the loop consisting of elements E , F and D to get

$$4 - v_6 + (-2) = 0 \Rightarrow v_6 = 2 \text{ V}$$

Check: The sum of the power supplied by all branches is

$$-(6)(2) - (-6)(-4) - (-4)(6) + (-2)(-3) + (4)(3) + (2)(-3) = -12 - 24 + 24 + 6 + 12 - 6 = 0$$

P3.3-6

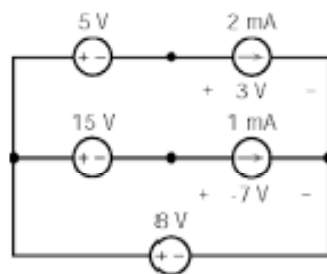


$$P_{2\text{mA}} = -[3 \times (2 \times 10^{-3})] = -6 \times 10^{-3} = -6 \text{ mW}$$

$$P_{1\text{mA}} = -[-7 \times (1 \times 10^{-3})] = 7 \times 10^{-3} = 7 \text{ mW}$$

(checked using LNAP 8/16/02)

P3.5-4

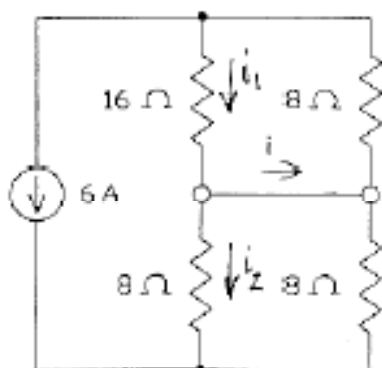


Current division:

$$i_1 = \frac{8}{16+8}(-6) = -2 \text{ A}$$


$$i_2 = \frac{8}{8+8}(-6) = -3 \text{ A}$$

$$i = i_1 - i_2 = \underline{+1 \text{ A}}$$

P3.7-1

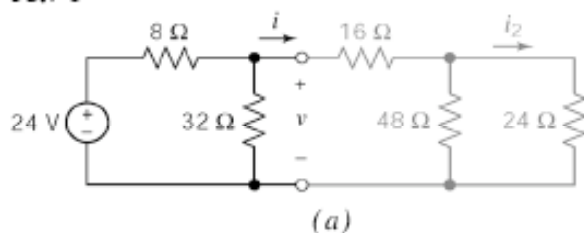

(a)

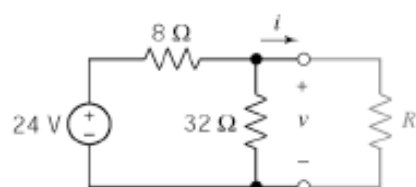

(b)

$$(a) R = 16 + \frac{48 \cdot 24}{48 + 24} = \underline{32 \Omega}$$




$$(b) v = \frac{\frac{32 \cdot 32}{32+32}}{8 + \frac{32 \cdot 32}{32+32}} 24 = \underline{16 \text{ V}};$$

$$i = \frac{16}{32} = \underline{\frac{1}{2} \text{ A}}$$




$$(c) i_2 = \frac{48}{48+24} \cdot \frac{1}{2} = \underline{\frac{1}{3} \text{ A}}$$

P3.7-3

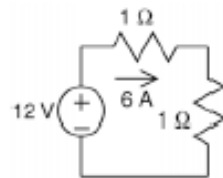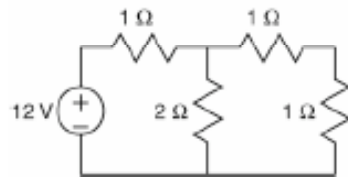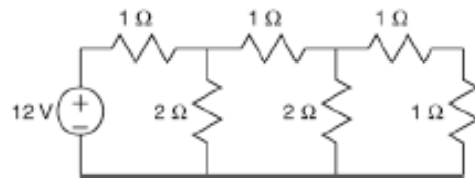Reduce the circuit from the right side by repeatedly replacing series $1\ \Omega$ resistors in parallel with a $2\ \Omega$ resistor by the equivalent $1\ \Omega$ resistor



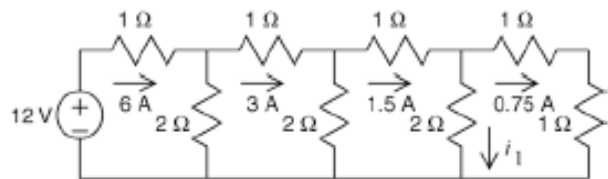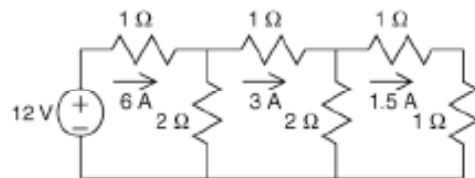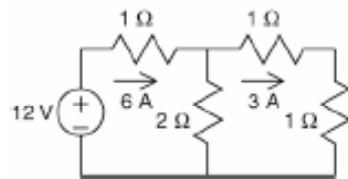This circuit has become small enough to be easily analyzed. The vertical $1\ \Omega$ resistor is equivalent to a $2\ \Omega$ resistor connected in parallel with series $1\ \Omega$ resistors:



$$i_1 = \frac{1+1}{2+(1+1)}(1.5) = 0.75\ \text{A}$$