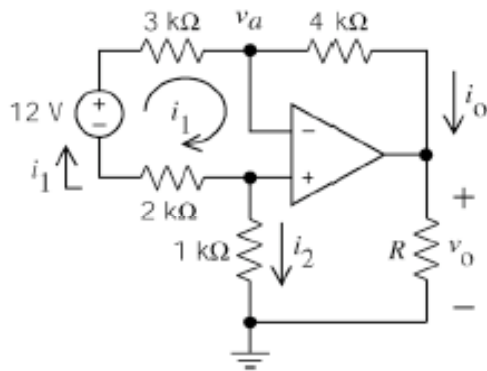


**P6.4-2**



Apply KVL to loop 1:

$$-12 + 3000 i_1 + 0 + 2000 i_1 = 0$$

$$\Rightarrow i_1 = \frac{12}{5000} = 2.4 \text{ mA}$$

The currents into the inputs of an ideal op amp are zero so

$$i_o = i_1 = 2.4 \text{ mA}$$

$$i_2 = -i_1 = -2.4 \text{ mA}$$


$$v_a = i_2(1000) + 0 = -2.4 \text{ V}$$

Apply Ohm's law to the 4 kΩ resistor

$$v_o = v_a - i_o(4000)$$

$$= -2.4 - (2.4 \times 10^{-3})(4000) = -12 \text{ V}$$

**P6.4-3**

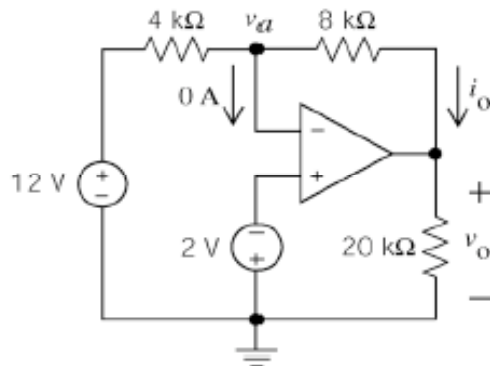

The voltages at the input nodes of an ideal op amp are equal so  $v_a = -2 \text{ V}$ .


Apply KCL at node  $a$ :

$$\frac{v_o - (-2)}{8000} + \frac{12 - (-2)}{4000} = 0 \Rightarrow v_o = -30 \text{ V}$$

Apply Ohm's law to the 8 kΩ resistor

$$i_o = \frac{-2 - v_o}{8000} = 3.5 \text{ mA}$$

**P6.5-1**

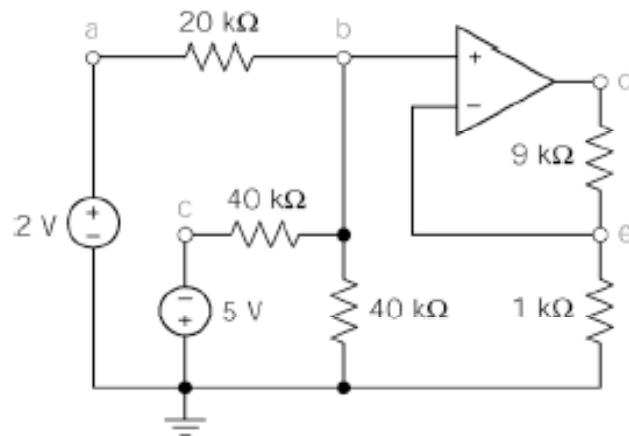


KCL at node b:  $\frac{v_b - 2}{20000} + \frac{v_b}{40000} + \frac{v_b + 5}{40000} = 0 \Rightarrow v_b = -\frac{1}{4} \text{ V}$

The node voltages at the input nodes of an ideal op amp are equal so  $v_c = v_b = -\frac{1}{4} \text{ V}$ .

KCL at node e:  $\frac{v_e}{1000} + \frac{v_e - v_d}{9000} = 0 \Rightarrow v_d = 10v_e = -\frac{10}{4} \text{ V}$

**P6.5-3**

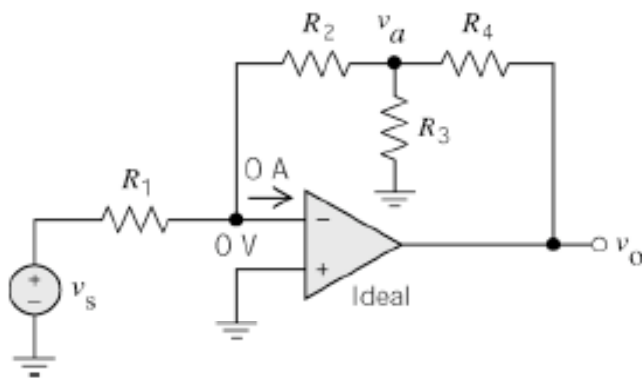

Apply KCL at the inverting input of the op amp:

$$-\left(\frac{v_a - 0}{R_2}\right) - \left(\frac{v_a - 0}{R_4}\right) = 0$$

$$\Rightarrow v_a = -\frac{R_2}{R_4} v_s$$

Apply KCL at node a:

$$\frac{v_a - v_o}{R_4} + \frac{v_a}{R_3} + \frac{v_a - 0}{R_2} = 0 \Rightarrow v_o = R_4 \left( \frac{1}{R_4} + \frac{1}{R_3} + \frac{1}{R_2} \right) v_a = \frac{R_2 R_3 + R_2 R_4 + R_3 R_4}{R_2 R_3} v_a$$

$$= -\frac{R_2 R_3 + R_2 R_4 + R_3 R_4}{R_1 R_3} v_s$$

Plug in values  $\Rightarrow$  yields  $\frac{v_o}{v_s} = -\frac{30+900+30}{4.8} = -200 \text{ V/V}$


**P6.5-4**

Ohm's law:


$$i = \frac{v_1 - v_2}{R_2}$$

KVL:
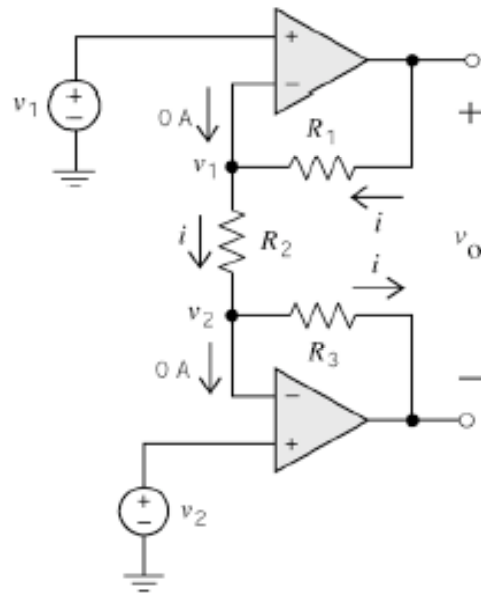
$$v_o = (R_1 + R_2 + R_3)i = \frac{R_1 + R_2 + R_3}{R_2}(v_1 - v_2)$$



**P6.5-6**

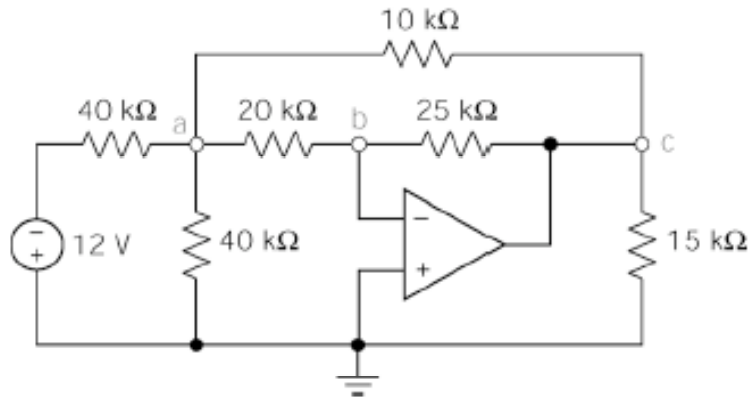

KCL at node b:

$$\frac{v_a}{20 \times 10^3} + \frac{v_c}{25 \times 10^3} = 0 \Rightarrow v_c = -\frac{5}{4}v_a$$

KCL at node a:

$$\frac{v_a - (-12)}{40 \times 10^3} + \frac{v_a}{10 \times 10^3} + \frac{v_a + 0}{20 \times 10^3} + \frac{v_a - \left(-\frac{5}{4}v_a\right)}{10 \times 10^3} = 0 \Rightarrow v_a = -\frac{12}{13} \text{ V}$$

So

$$v_c = -\frac{5}{4}v_a = -\frac{15}{13}$$