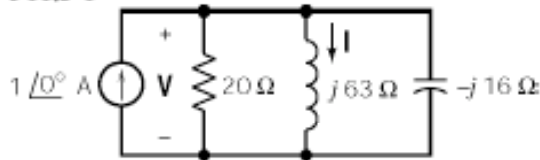


P11.3-1




$$1\angle 0^\circ = \frac{V}{20} + \frac{V}{j63} + \frac{V}{-j16} \Rightarrow V = 14.6\angle -43^\circ \text{ V}$$

$$I = \frac{V}{j63} = 0.23\angle -133^\circ \text{ A}$$

$$\begin{aligned} p(t) &= i(t)v(t) = 0.23(\cos(2\pi \cdot 10^3 t - 133^\circ)) \times 14.6 \cos(2\pi \cdot 10^3 t - 43^\circ) \\ &= 3.36 \cos(2\pi \cdot 10^3 t - 133^\circ) \cos(2\pi \cdot 10^3 t - 43^\circ) \\ &= 1.68 (\cos(90^\circ) + \cos(4\pi \cdot 10^3 t - 176^\circ)) \\ &= 1.68 \cos(4\pi \cdot 10^3 t - 176^\circ) \end{aligned}$$

P11.3-2

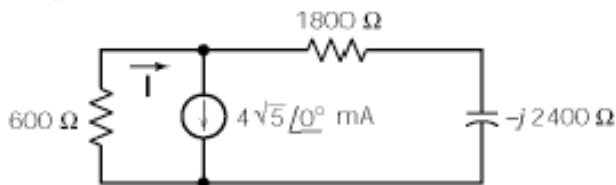


Current division:

$$\begin{aligned} I &= 4\sqrt{5} \left[\frac{1800 - j2400}{1800 - j2400 + 600} \right] \\ &= 5\sqrt{\frac{5}{2}} \angle -8.1^\circ \text{ mA} \end{aligned}$$

$$P_{600\Omega} = \frac{|I|^2 600}{2} = 300(25) \left(\frac{5}{2} \right) = 1.875 \times 10^4 \mu\text{W} = 18.75 \text{ mW}$$

$$P_{\text{source}} = \frac{|V||I|\cos\theta}{2} = \frac{1}{2}(600) \left(5\sqrt{\frac{5}{2}} \right) (4\sqrt{5}) \cos(-8.1^\circ) = 2.1 \times 10^4 \mu\text{W} = 21 \text{ mW}$$


P11.3-3

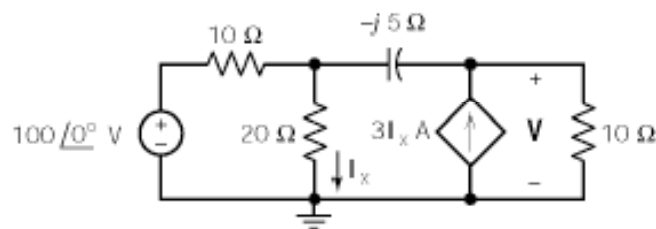

P11.5-1

$$I^* = \frac{2 \text{ S}}{12\angle 0^\circ} = \frac{2(3.6 + j7.2)}{12\angle 0^\circ} = 0.6 + j1.2 = 1.342\angle 63.43^\circ \text{ A}$$

$$R + j4L = \frac{12\angle 0^\circ}{1.342\angle -63.43^\circ} = 8.94\angle 63.43^\circ = 4 + j8 \Rightarrow R = 4 \text{ } \Omega \text{ and } L = 2 \text{ H}$$

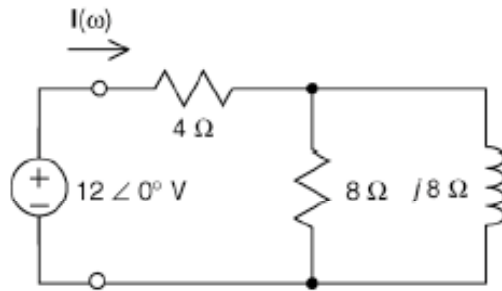P11.5-3

Let

$$\mathbf{Z}_p = \frac{8(j8)}{8+j8} = \frac{j8}{1+j} \times \frac{1-j}{1-j} = \frac{8+j8}{2} = 4+j4 \text{ } \Omega$$

Next

$$\mathbf{I} = \frac{12\angle 0^\circ}{4+\mathbf{Z}_p} = \frac{12\angle 0^\circ}{4+(8+j8)} = 1.342\angle -26.6^\circ \text{ A}$$

Finally

$$\mathbf{S} = \frac{(12\angle 0^\circ)(1.342\angle -26.6^\circ)^*}{2} = 7.2 + j3.6 \text{ VA}$$

P11.8-1

$$\mathbf{Z}_i = 4000 \parallel -j2000 = 800 - j1600 \ \Omega$$

$$\mathbf{Z}_L = \mathbf{Z}_i^* = 800 + j1600 \ \Omega$$

$$R + j1000L = 800 + j1600 \Rightarrow \begin{cases} R=800 \ \Omega \\ L=1.6 \ \text{H} \end{cases}$$

P11.8-2

$$\mathbf{Z}_i = 25,000 \parallel -j50,000 = 20,000 - j10,000 \ \Omega$$

$$\mathbf{Z}_L = \mathbf{Z}_i^* = 20,000 + j10,000 \ \Omega$$

$$R + j\omega L = 20,000 + j10,000 \Rightarrow \begin{cases} R=20 \ \text{k}\Omega \\ 100L=10,000 \\ L=100 \ \text{H} \end{cases}$$

After selecting these values of R and L ,

$$|\mathbf{i}| = 1.4 \ \text{mA} \ \text{and} \ P_{\max} = \left(\frac{0.14 \times 10^{-2}}{\sqrt{2}} \right)^2 (20 \times 10^3) = 19.5 \ \text{mW}$$

Since $P_{\max} > 12 \ \text{mW}$, yes, we can deliver 12 mW to the load.

P11.8-3

$$\mathbf{Z}_i = 800 + j1600 \ \Omega \ \text{and} \ \mathbf{Z}_L = \frac{R \left(\frac{-j}{\omega C} \right)}{R - \frac{j}{\omega C}} = \frac{R - j\omega R^2 C}{1 + (\omega RC)^2}$$

$$\mathbf{Z}_L = \mathbf{Z}_i^* \Rightarrow \frac{R \left(\frac{-j}{\omega C} \right)}{R - \frac{j}{\omega C}} = \frac{R - j\omega R^2 C}{1 + (\omega RC)^2} = 800 - j1600 \ \Omega$$

Equating the real parts gives

$$800 = \frac{R}{1 + (\omega RC)^2} = \frac{4000}{1 + [(5000)(4000)C]^2} \Rightarrow C = 0.1 \ \mu\text{F}$$